

Faculty of Science
B.Sc. III-Year, CBCS-V Semester Examinations, 2018-19
Skill Enhancement Course
PAPER: COMPUTER ORGANIZATION

Time: 2 Hours

Max Marks: 40

Section-A

- I. Answer any two of the following questions (2x5=10 Marks)
1. Explain register and shift registers.
 2. Explain gated SR latch.
 3. Differentiate between the circuits designed by ROMs and PLAs.
 4. Design a circuit to perform the multiplication of two binary numbers.

Section-B

- II. Answer the following questions (2x15=30 Marks)
5. (a) Discuss in detail about J-K Flip Flops.
(OR)
(b) Discuss in detail about D- Flip Flops.
 6. (a) Explain Decoders with suitable example
(OR)
(b) What is Sequential Circuit? Explain UP/DOWN Counter with an example.
